

Multiplication

Multiplication = series of additions:

1. align first operand (*multiplicand*) with i^{th} digit of second operand (*multiplier*)

2. add shifted multiplicand n times to result (n = value of the multiplier digit)

3. repeat 1. and 2. for all multiplier digits i

4. $n\text{-digit} \times n\text{-digit} = \underline{2n\text{-digit}}$ result
- binary system \Rightarrow either 0 or 1
 - problem is reduced to *add/noadd*

Example (decimal): $6 \times 13 = 78$

0 6

$\times 13$

1 8

$+ 06$

0 0 7 8

Multiplicand

Multiplier

03×06

10×06

Product

Example (binary): $6 \times 13 = 78$

0 1 1 0

$\times 1101$

0 1 1 0

0 0 0 0

0 1 1 0

$+ 0110$

0 1 1 0 0 0 0 0

0 1 0 0 1 1 1 0

Multiplicand

Multiplier

0001×0110

0000×0110

0100×0110

1000×0110

(carry)

Product

Multiplication Circuitry

1. Complete logical network:
- direct and fast implementation
 - large number ($n \times n$) of full adders
 - potentially complex circuitry
- Ripple-Carry:** most intuitive realization

\Rightarrow rippling per *row*

\Rightarrow feed last carry to MSB of next row
- Carry-Save:** three rows at once

\Rightarrow create separate *Carry* & *Sum* vectors

\Rightarrow add up later

\Rightarrow tree-like structure results

Figures 6.16–6.19 in the book

Multiplication Circuitry

2. Sequential shift/add multiplication:
- involves less circuitry
 - uses single adder unit only
 - result is developed in a shift register
 - requires sequencing control \Rightarrow *slow!*
3. Software multiplication:
- no extra circuitry
 - subroutine solving multiplication
 - loop with shift/rotate/add instructions
 - requires several instructions \Rightarrow *slowest!*

Multiplication Circuitry

- Signed multiplicands?

- how to handle in partial products?

\Rightarrow sign extension
- Optimization?

- reduce carry-over impacts
 - reduce number of partial products

\Rightarrow Booth recoding

\Rightarrow bit pairing

next time...

Multiplication: $6 \times 13 = 78$

Sequential addition from row to row:

$ \begin{array}{r} 0110 \\ \times 1101 \\ \hline 0110 \\ 0000 \\ 0110 \\ + 0110 \\ \hline 01001110 \end{array} $	<p>Sum:</p> <p>0000110 0000110 0001110 0100110 Product</p>
--	--


238

Sequential Shift/Add-Method

- Method to avoid adder arrays
- shift register for partial product and multiplier
- with each cycle,
 1. partial product increases by one digit
 2. multiplier is reduced by one digit
- MSBs of partial product and multiplicand are aligned in each cycle
- not the multiplicand is shifted
 \Rightarrow partial product and multiplier are shifted together


239

Example 1: $6 \times 13 = 78$

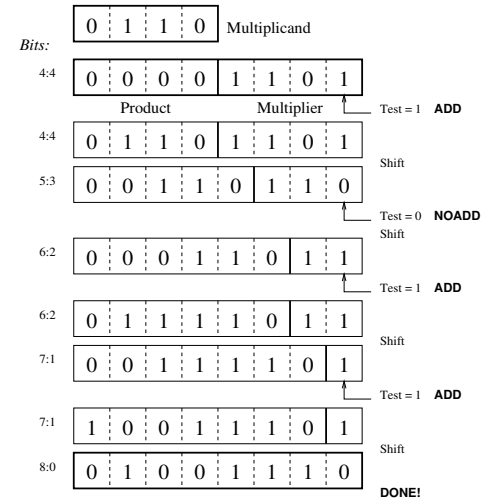

240

Example 2: $15 \times 13 = 195$

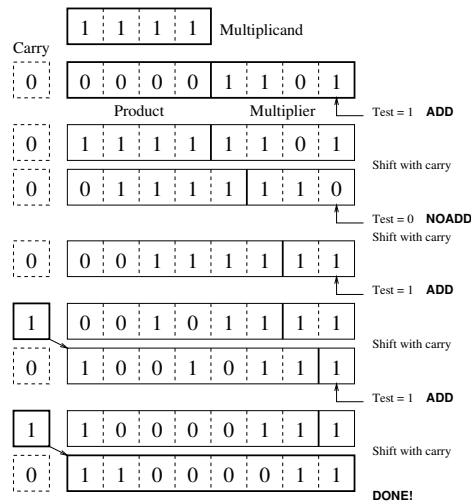

241

Sequential Shift/Add-Method

1. Load multiplier into *lower* half of shift register (the *upper* half is to be zeroed)
 2. test LSB of the shift register
 3. if LSB is set
 - then add multiplicand to the *upper* half of the shift register
 - else add nothing (make sure carry-bit is cleared!)
 4. perform right shift including carry on full shift register
 5. repeat from 2. as long as multiplier part of shift register is not empty
 6. after termination, the shift register (both halves!) contains the product
- Easy to implement in software

242